

TERMS USE

Copyright 2016 The Science Penguin Incorporated

All rights reserved by author.

Permission to copy for single classroom use only.

Not for public display.

Redistributing, editing, selling, or posting this item or any part thereof on the Internet is strictly prohibited.

Placing any part of this product on the Internet is a violation of the Digital Millennium Copyright Act (DMCA).


You may reproduce pages for single classroom use only.

Fonts and
Graphics:




CIRCUIT CUT AND PASTE

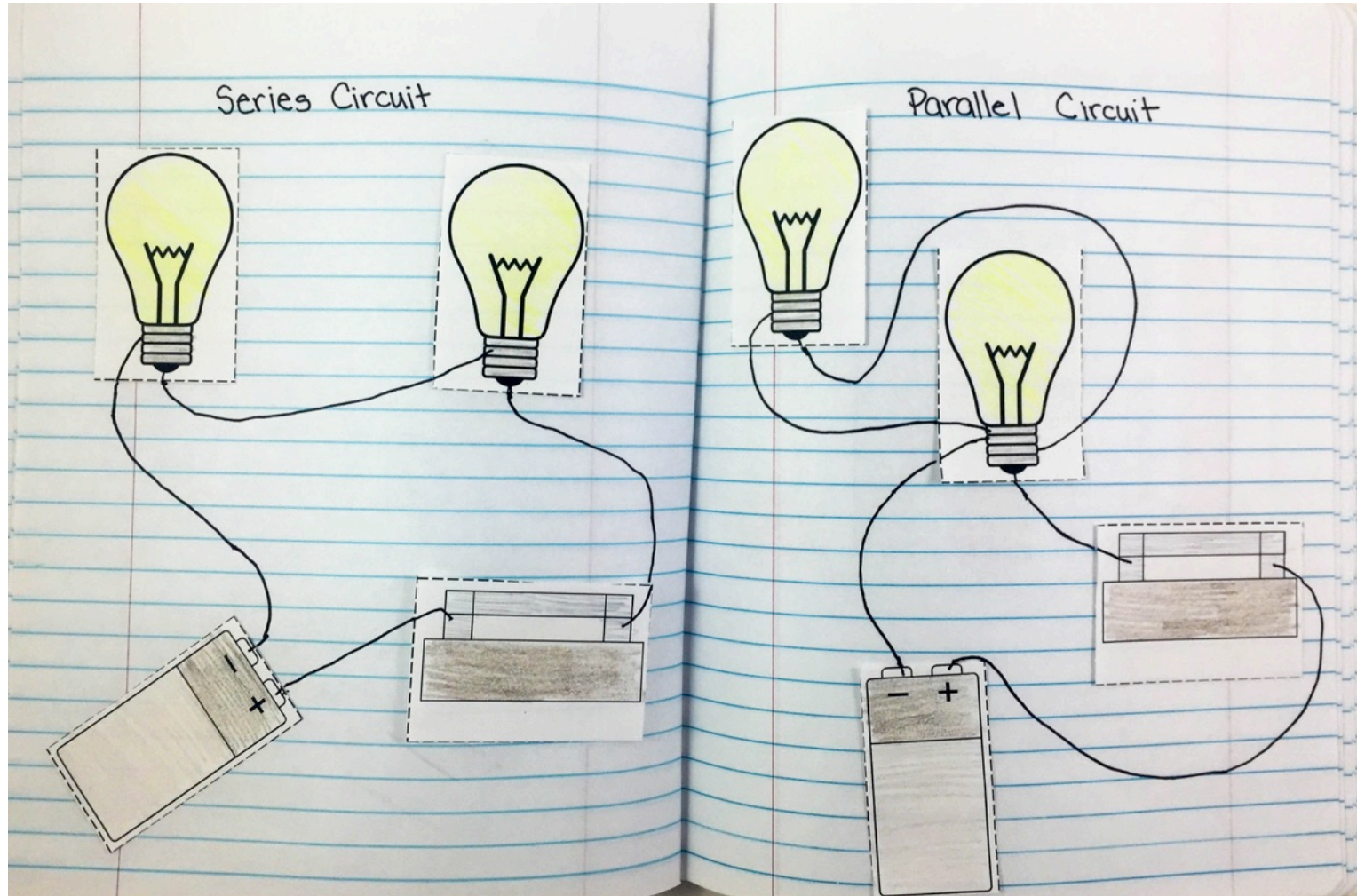Cut out the pieces. Place them in your journal to create a working parallel and series circuit. Glue the pieces down and draw the wires. Recommended Reflection Prompt: Draw another example of how both a series circuit circuit and parallel circuit may be set up.



CIRCUIT CUT AND PASTE

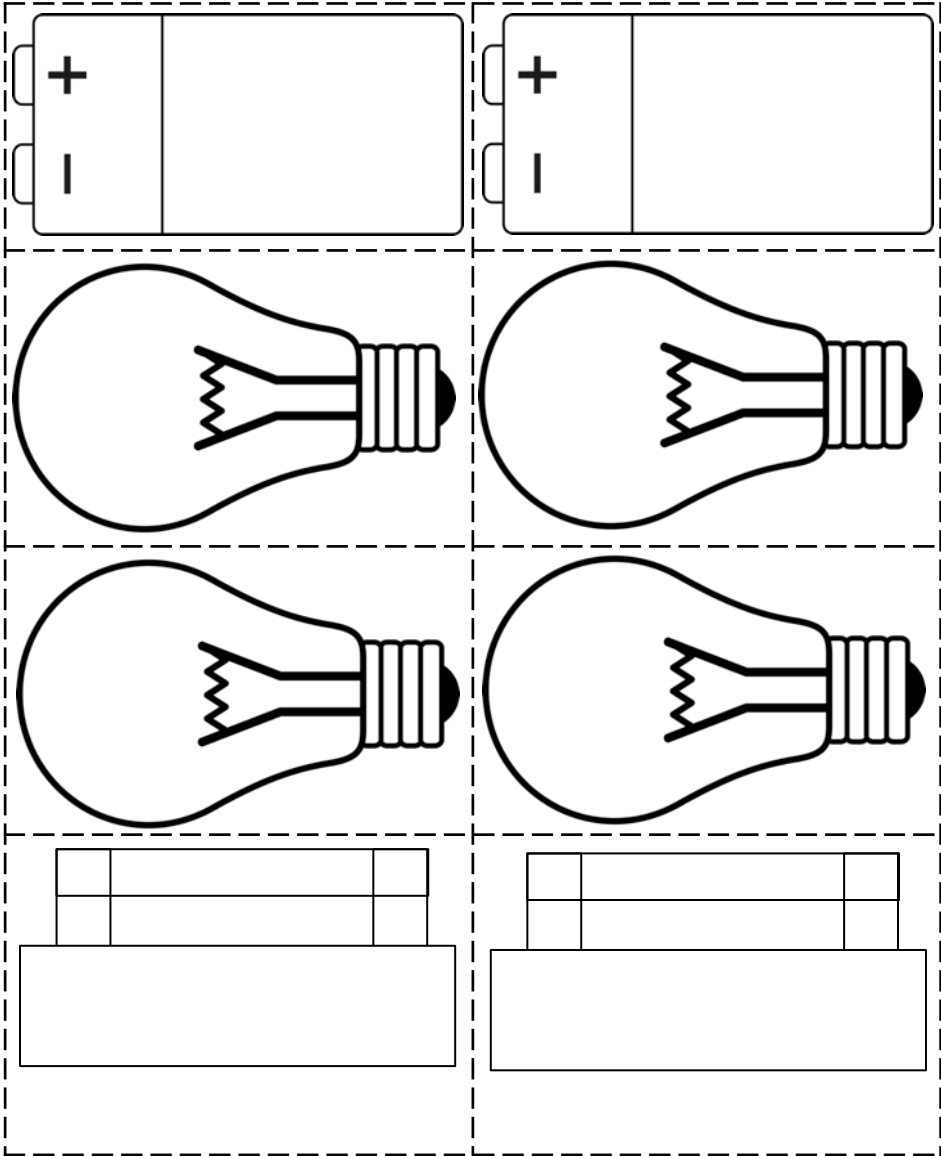

CIRCUIT CUT AND PASTE

